

LM2623 General Purpose, Boost Converter Circuit


National Semiconductor
Application Note 1221
John Fairbanks
February 2004



The next page shows the generic application circuit for LM2623 boost converters. The LM2623 boost converter circuits are very conventional, except for the ratio adaptive circuitry that is used to change the duty cycle. These components adjust the duty cycle to match it to the input/output voltage ratio requirements. R3 provides the drive current for the oscillator (frequency increases with lower resistance values). C3 and R5 provide the duty cycle adjustment. The default duty cycle when C3 and R5 are left out is about 17%. The value of C3 generally determines the total amount of charge transfer and resulting duty cycle adjustment. Smaller R3 values require larger C3 values (more charge transfer) to achieve the same duty cycle adjustment percentage. When more than 17% is necessary and it is not necessary to adjust the duty cycle dynamically (as the input to output voltage ratio changes), R5 can be omitted. Adding R5 allows the duty cycle to change as the input to output voltage ratio changes due to the battery discharging in portable applications. In applications where the fresh or fully charged battery voltage is close to the output voltage (2 cells generating 3.3V), the optimum duty cycle changes dramatically as the battery discharges. Use of the correct R5 in these situations will optimize the duty cycle for the voltage ratio and minimize the ripple due to overshoot caused by stored energy in the coil.

The table of values below the application circuit on the bottom of this page should produce good performance for the application requirements stated. Recommended inductor values are based on input voltage, load current and operating frequency. 4.7 μH works well in most LM2623 two cell applications. 6.8 μH works well in most LM2623 Lilon or three cell applications. RF1 and RF2 set the output voltage by dividing the output voltage for comparison to the reference at the pin 4 FB pin. CF1 couples the AC ripple from the output directly into the comparator at pin 4. When in regulation, this triggers the regulation limit each switching cycle. Triggering this limit allows the comparator to make the voltage comparison from the same direction (above the limit) each switching cycle. This minimizes the hysteretic component of ripple. A 68 μF or larger output capacitor is recommended to minimize ripple resulting from overshoot due to stored energy in the coil. The rectifier diode should be selected as a function of peak currents and efficiency requirements.

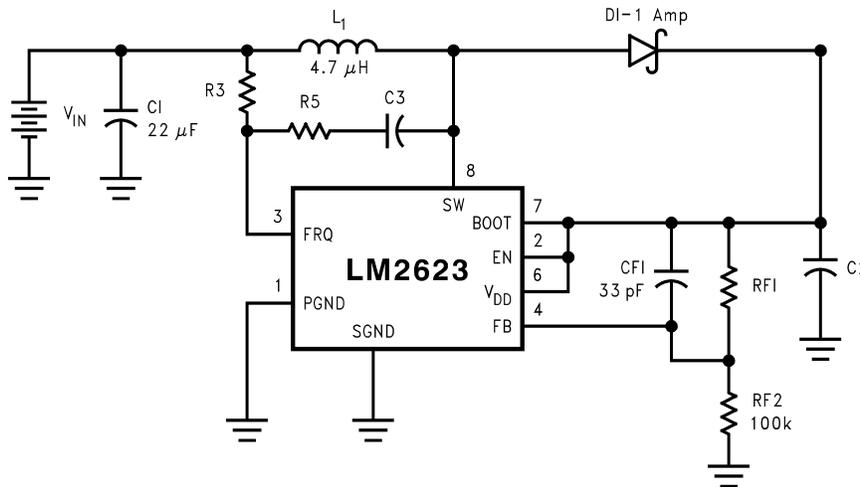LM2623 Boost Converter Circuit
Typical Applications
Digital Cameras



20039401

V_{IN}	Load Type	V_{OUT}	RF1	R3	R5	C3	C2
2 Cells	Analog/Digital	3.6V	182k	90k	35k	3.3 pF	100 μF Tant + 4.7 μF Cer
2 Cells	Motor Drive	5V	300k	90k	22k	4.7 pF	68 μF Tant
3 Cells or Li I	Motor Drive	5V	300k	150k	35k	4.7 pF	68 μF Tant

Notes

LIFE SUPPORT POLICY

NATIONAL'S PRODUCTS ARE NOT AUTHORIZED FOR USE AS CRITICAL COMPONENTS IN LIFE SUPPORT DEVICES OR SYSTEMS WITHOUT THE EXPRESS WRITTEN APPROVAL OF THE PRESIDENT AND GENERAL COUNSEL OF NATIONAL SEMICONDUCTOR CORPORATION. As used herein:

1. Life support devices or systems are devices or systems which, (a) are intended for surgical implant into the body, or (b) support or sustain life, and whose failure to perform when properly used in accordance with instructions for use provided in the labeling, can be reasonably expected to result in a significant injury to the user.
2. A critical component is any component of a life support device or system whose failure to perform can be reasonably expected to cause the failure of the life support device or system, or to affect its safety or effectiveness.

BANNED SUBSTANCE COMPLIANCE

National Semiconductor certifies that the products and packing materials meet the provisions of the Customer Products Stewardship Specification (CSP-9-111C2) and the Banned Substances and Materials of Interest Specification (CSP-9-111S2) and contain no "Banned Substances" as defined in CSP-9-111S2.



National Semiconductor
Americas Customer
Support Center
Email: new.feedback@nsc.com
Tel: 1-800-272-9959

www.national.com

National Semiconductor
Europe Customer Support Center
Fax: +49 (0) 180-530 85 86
Email: europe.support@nsc.com
Deutsch Tel: +49 (0) 69 9508 6208
English Tel: +44 (0) 870 24 0 2171
Français Tel: +33 (0) 1 41 91 8790

National Semiconductor
Asia Pacific Customer
Support Center
Email: ap.support@nsc.com

National Semiconductor
Japan Customer Support Center
Fax: 81-3-5639-7507
Email: jpn.feedback@nsc.com
Tel: 81-3-5639-7560